

# Digital Systems : Assignment2

*Nimitt (22110169)*

*Pratham Sharda (22110203)*

This document demonstrates the Assignment 2 of the Digital Systems course.

## Port Names

### 1 Bit Adder

Module Name : FullAdder

1. A : First Number
2. B : Second Number
3. Cin : Carry in
4. Sum, Cout

### 8 Bit Adder/ Subtractor

Module Name : AdderSubtractor8b

1. A : 8 Bit First Number
2. B : 8 Bit Second Number
3. OUT : 8 bit Answer ( Sum/ Difference)
4. Cout : Carry overflow

### Gray Converter

1. A : 9 Bit Number
2. OUT : 9 Bit Output

### Combined :

1. A : First 8 bit Number

2. B : Second No
3. OUT : Final Output

## 1 Bit Full Adder

First, we implement the 1 bit Full Adder :

```
Full Adder
`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company:
// Engineer:
//
// Create Date: 01/21/2024 09:07:38 AM
// Design Name:
// Module Name: FullAdder
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
/////////////////////////////////////////////////////////////////

module FullAdder(
    input A,
    input B,
    input Cin,
    output Sum,
    output Cout
```

```

    );
    and a1(f, Cin,A);
    and a2(g, A, B);
    and a3(h, B, Cin);
    or a4(Cout, f, g, h);

    xor a5(i, A, B);
    xor a6(Sum,i,Cin);

endmodule

```

```

TestBench for full Adder
`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company:
// Engineer:
//
// Create Date: 01/21/2024 10:18:59 AM
// Design Name:
// Module Name: FullAdder_tb
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
/////////////////////////////////////////////////////////////////

module FullAdder_tb();

```


```

reg A, B, Cin;
wire Sum, Cout;
FullAdder uut(A, B, Cin, Sum, Cout);
initial begin
A = 0; B = 0; Cin = 0;
#10;
A = 1; B = 0; Cin = 0;
#10;
A = 1; B = 0; Cin = 1;
#10;
A = 0; B = 0; Cin = 1;
#10;
A = 1; B = 0; Cin = 0;
#10;
A = 1; B = 1; Cin = 1;
#10;

$finish();
end
endmodule

```

Simulation Results :

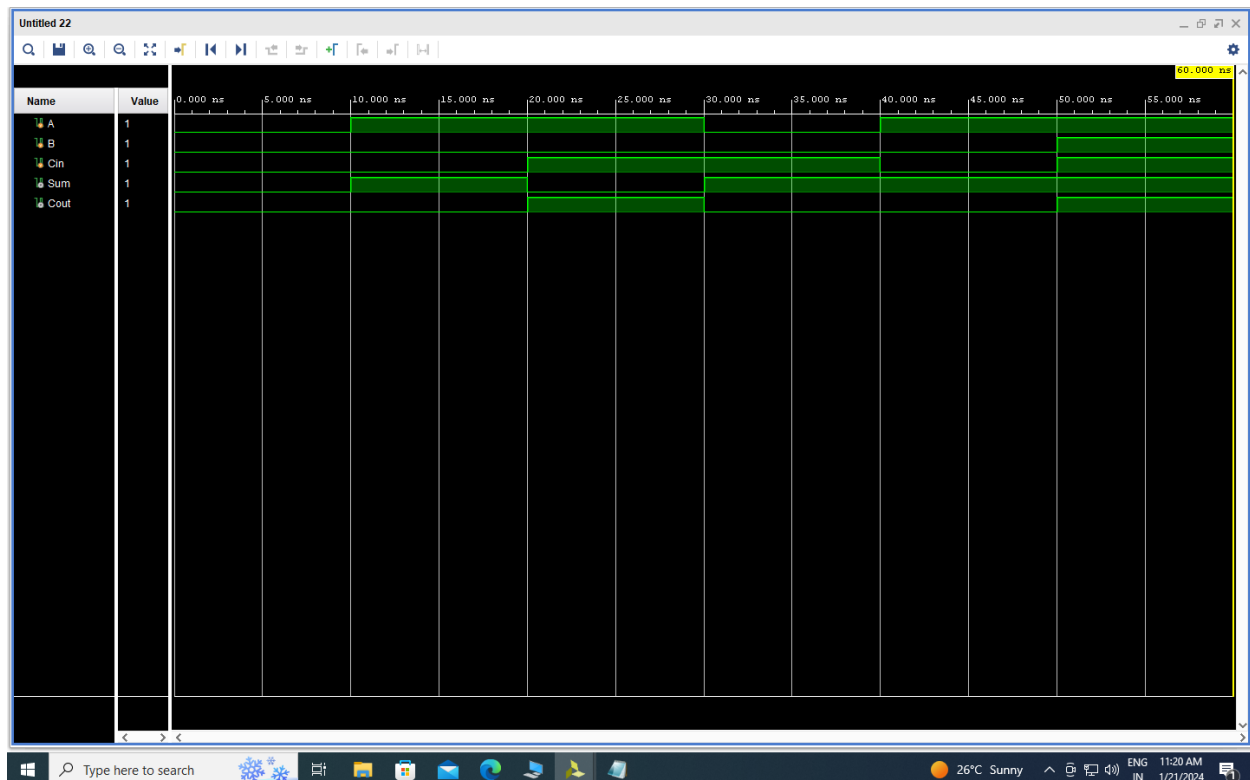

Clearly, Simulation shows the expected output.

## 8 Bit Adder Subtractor

Now, we implement 8 Bit Adder Subtractor using the Full Adder module :

```

adder_subtractor
`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company:
// Engineer:
//
// Create Date: 01/21/2024 09:13:45 AM
// Design Name:
// Module Name: AdderSubtractor8b
// Project Name:
// Target Devices:

```

```

// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
////////////////////////////////////

module AdderSubtractor8b(
    input [7:0] A,
    input [7:0] B,
    input Mode,
    output [7:0] OUT,
    output Cout
);
    wire [7:0] Cout1;
    wire [7:0] Cout2;
    wire [7:0] B_;
    wire [7:0] B__;
    wire [7:0] Bf;
    wire [7:0] one;

    not n1(B_[0], B[0]);
    not n2(B_[1], B[1]);
    not n3(B_[2], B[2]);
    not n4(B_[3], B[3]);
    not n5(B_[4], B[4]);
    not n6(B_[5], B[5]);
    not n7(B_[6], B[6]);
    not n8(B_[7], B[7]);

```

```

FullAdder FA1_ (.A(1), .B(B_[0]), .Cin(0), .Sum(B__[0]), .Cout1[0]);
FullAdder FA2_ (.A(0), .B(B_[1]), .Cin(Cout1[0]), .Sum(B__[1]), .Cout1[1]);
FullAdder FA3_ (.A(0), .B(B_[2]), .Cin(Cout1[1]), .Sum(B__[2]), .Cout1[2]);
FullAdder FA4_ (.A(0), .B(B_[3]), .Cin(Cout1[2]), .Sum(B__[3]), .Cout1[3]);
FullAdder FA5_ (.A(0), .B(B_[4]), .Cin(Cout1[3]), .Sum(B__[4]), .Cout1[4]);
FullAdder FA6_ (.A(0), .B(B_[5]), .Cin(Cout1[4]), .Sum(B__[5]), .Cout1[5]);
FullAdder FA7_ (.A(0), .B(B_[6]), .Cin(Cout1[5]), .Sum(B__[6]), .Cout1[6]);
FullAdder FA8_ (.A(0), .B(B_[7]), .Cin(Cout1[6]), .Sum(B__[7]), .Cout1[7]);

```

```

assign Bf = (Mode == 0) ? B : B__;

```

```

FullAdder FA1 (.A(A[0]), .B(Bf[0]), .Cin(0), .Sum(OUT[0]), .Cout2[0]);
FullAdder FA2 (.A(A[1]), .B(Bf[1]), .Cin(Cout2[0]), .Sum(OUT[1]), .Cout2[1]);
FullAdder FA3 (.A(A[2]), .B(Bf[2]), .Cin(Cout2[1]), .Sum(OUT[2]), .Cout2[2]);
FullAdder FA4 (.A(A[3]), .B(Bf[3]), .Cin(Cout2[2]), .Sum(OUT[3]), .Cout2[3]);
FullAdder FA5 (.A(A[4]), .B(Bf[4]), .Cin(Cout2[3]), .Sum(OUT[4]), .Cout2[4]);
FullAdder FA6 (.A(A[5]), .B(Bf[5]), .Cin(Cout2[4]), .Sum(OUT[5]), .Cout2[5]);
FullAdder FA7 (.A(A[6]), .B(Bf[6]), .Cin(Cout2[5]), .Sum(OUT[6]), .Cout2[6]);
FullAdder FA8 (.A(A[7]), .B(Bf[7]), .Cin(Cout2[6]), .Sum(OUT[7]), .Cout2[7]);

```

```

assign Cout = (Mode == 0) ? Cout2[7] : ~Cout2[7];

```

```

endmodule

```

TestBench Adder Subtractor

```

`timescale 1ns / 1ps

```

```

////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////

```

```

// Company:

```

```

// Engineer:

```

```

//

```

```

// Create Date: 01/21/2024 10:12:41 AM

```


```
// Design Name:
// Module Name: AdderSubtractor8b_tb
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
////////////////////////////////////
```

```
module AdderSubtractor8b_tb();
    reg [7:0] A;
    reg [7:0] B;
    reg Mode;
    wire [7:0] OUT;
    wire Cout;
    AdderSubtractor8b uut(A, B, Mode, OUT, Cout);
    initial
    begin
        A = 8'b00000001; B = 8'b00000001; Mode = 0;
        #10;
        A = 8'b00000001; B = 8'b00000001; Mode = 1;
        #10;
        A = 8'b00000011; B = 8'b00000001; Mode = 0;
        #10;
        A = 8'b00000011; B = 8'b00000001; Mode = 1;
        #10;
        A = 8'b00000011; B = 8'b10000001; Mode = 1;
        #10;
        $finish();
    end
endmodule
```



```
end
endmodule
```

Simulation Results :

 

We can see the module has been implemented correctly.

## Gray Code Converter

Now, we move on to building the 9 Bit gray code converter :

```
Gray Converter
`timescale 1ns / 1ps
////////////////////////////////////
// Company:
// Engineer:
//
```

```
// Create Date: 01/21/2024 09:18:01 AM
// Design Name:
// Module Name: GrayConverter
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
////////////////////////////////////
```

```
module GrayConverter(
    input [9:0] A,
    output [9:0] OUT
);
    assign OUT[8] = A[8];
    xor a1(OUT[7], A[8], A[7]);
    xor a2(OUT[6], A[7], A[6]);
    xor a3(OUT[5], A[6], A[5]);
    xor a4(OUT[4], A[5], A[4]);
    xor a5(OUT[3], A[4], A[3]);
    xor a6(OUT[2], A[3], A[2]);
    xor a7(OUT[1], A[2], A[1]);
    xor a8(OUT[0], A[1], A[0]);
endmodule
```

```
`timescale 1ns / 1ps
////////////////////////////////////
// Company:
```

```
// Engineer:
//
// Create Date: 01/21/2024 10:07:19 AM
// Design Name:
// Module Name: GreyConverter_tb
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
////////////////////////////////////,
```


```
module GreyConverter_tb();
    reg [8:0] A;
    wire [8:0] OUT;
    GrayConverter uut(A, OUT);
    initial
    begin
        A = 9'b000000001;
        #10;
        A = 9'b000000010;
        #10;
        A = 9'b000000011;
        #10;
        A = 9'b100000001;
        #10;
        A = 9'b000000010;
        #10;
        A = 9'b010000011;
```

```

#10;
A = 9'b0000010001;
#10;
A = 9'b0000000010;
#10;
A = 9'b0000001011;
#10;
$finish();
end
endmodule

```

Simulation Results :

 

Simulation results are as expected.

## Combined Adder Subtractor Gray Converter

Now, we combine 8 Bit adder subtractor and gray converter to implement the final module

## Combined Adder Subtractor Gray Converter

```
`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company:
// Engineer:
//
// Create Date: 01/21/2024 09:21:13 AM
// Design Name:
// Module Name: Combined
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
/////////////////////////////////////////////////////////////////

module Combined(
    input [7:0] A,
    input [7:0] B,
    input Mode,
    output [8:0] OUT
);
    wire Cout;
    wire [7:0] adderOut;
    wire [8:0] adderOut9;
    AdderSubtractor8b a1(.A(A), .B(B), .Mode(Mode), .OUT(adderOut));
    assign adderOut9[7:0] = adderOut;
    assign adderOut9[8] = Cout;
```

```

        GrayConverter g1(.A(adderOut9), .OUT(OUT));

endmodule

```

TestBench

```
`timescale 1ns / 1ps
```

```
////////////////////////////////////////////////////////////////
```

```
// Company:
```

```
// Engineer:
```

```
//
```

```
// Create Date: 01/21/2024 09:55:00 AM
```

```
// Design Name:
```

```
// Module Name: Combined_tb
```

```
// Project Name:
```

```
// Target Devices:
```

```
// Tool Versions:
```

```
// Description:
```

```
//
```

```
// Dependencies:
```

```
//
```

```
// Revision:
```

```
// Revision 0.01 - File Created
```

```
// Additional Comments:
```

```
//
```

```
////////////////////////////////////////////////////////////////
```

```
module Combined_tb();
```

```
    reg [7:0] A;
```

```
    reg [7:0] B;
```

```
    reg Mode;
```

```
    wire [8:0] OUT;
```

```
    Combined uut( A, B, Mode, OUT);
```

```
    initial
```

```
    begin
```


```

A = 8'b00000001; B = 8'b00000001; Mode = 0;
#10;
A = 8'b00000001; B = 8'b00000001; Mode = 1;
#10;
A = 8'b00000011; B = 8'b00000001; Mode = 0;
#10;
A = 8'b00000011; B = 8'b00000001; Mode = 1;
#10;
A = 8'b00100001; B = 8'b00000001; Mode = 0;
#10;
A = 8'b00000001; B = 8'b00000001; Mode = 1;
#10;
A = 8'b10000011; B = 8'b10000001; Mode = 0;
#10;
A = 8'b00100011; B = 8'b01000001; Mode = 1;
#10;

$finish();
end
endmodule

```

Simulation Results :

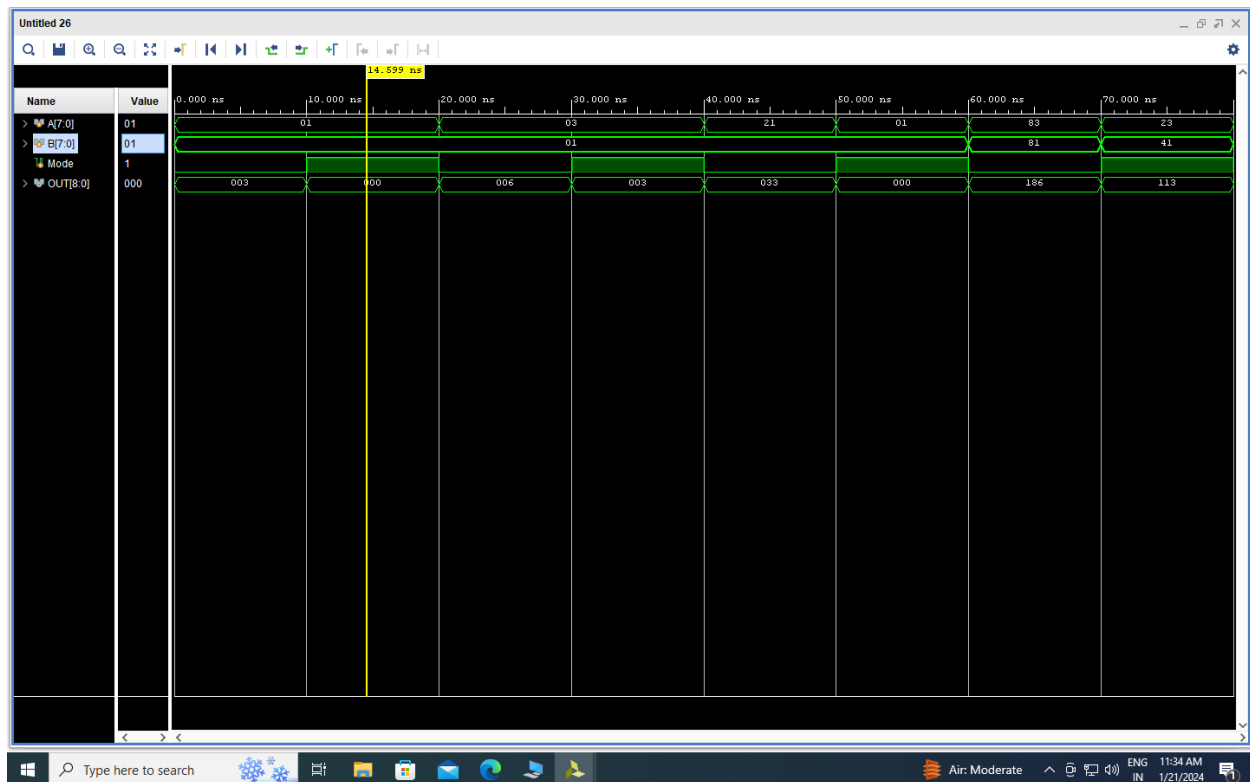

We can see the final module works correctly. This concludes the documentation.