

Digital Systems : LAB 4

Pratham Sharda (22110203)

Nimitt (22110169)

a. Array Multiplier

```
`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company:
// Engineer:
//
// Create Date: 02/17/2024 01:19:26 PM
// Design Name:
// Module Name: array_multiplier
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
/////////////////////////////////////////////////////////////////

module array_multiplier(
    input [7:0] A,
    input [7:0] B,
    output reg [15:0] OUT
);
```

```

reg [15:0] temp;
parameter n = 8;
parameter l = 16;
integer i = 0;
integer j = 0;

always @(*)
begin
    OUT = 0;
    for (i = 0; i < n; i=i+1)
        for (j = 0; j < i+1; j=j+1)
            begin
                temp = 0;
                temp[i] = (A[i-j] & B[j]);
                OUT = OUT + temp;
            end

    for (i = n; i < l; i=i+1)
        for (j = n - 1; j > i-n; j=j-1)
            begin
                temp = 0;
                temp[i] = (A[i-j] & B[j]);
                OUT = OUT + temp;
            end
        end
    end
endmodule

```

```

TestBench
module array_multiplier_tb();
    reg [7:0] A;
    reg [7:0] B;
    wire [15:0] OUT;

    array_multiplier uut(A,B,OUT);


```

```


A = 1; B = 1;
#10;
A = 10; B = 23;
#10;
A = 20; B = 4;
#10;
A = 127; B = 5;
#10;
A = 8; B = 45;
#10;
A = 85; B = 100;
#10;
A = 34; B = 121;
#10;
endmodule

```

Schematic

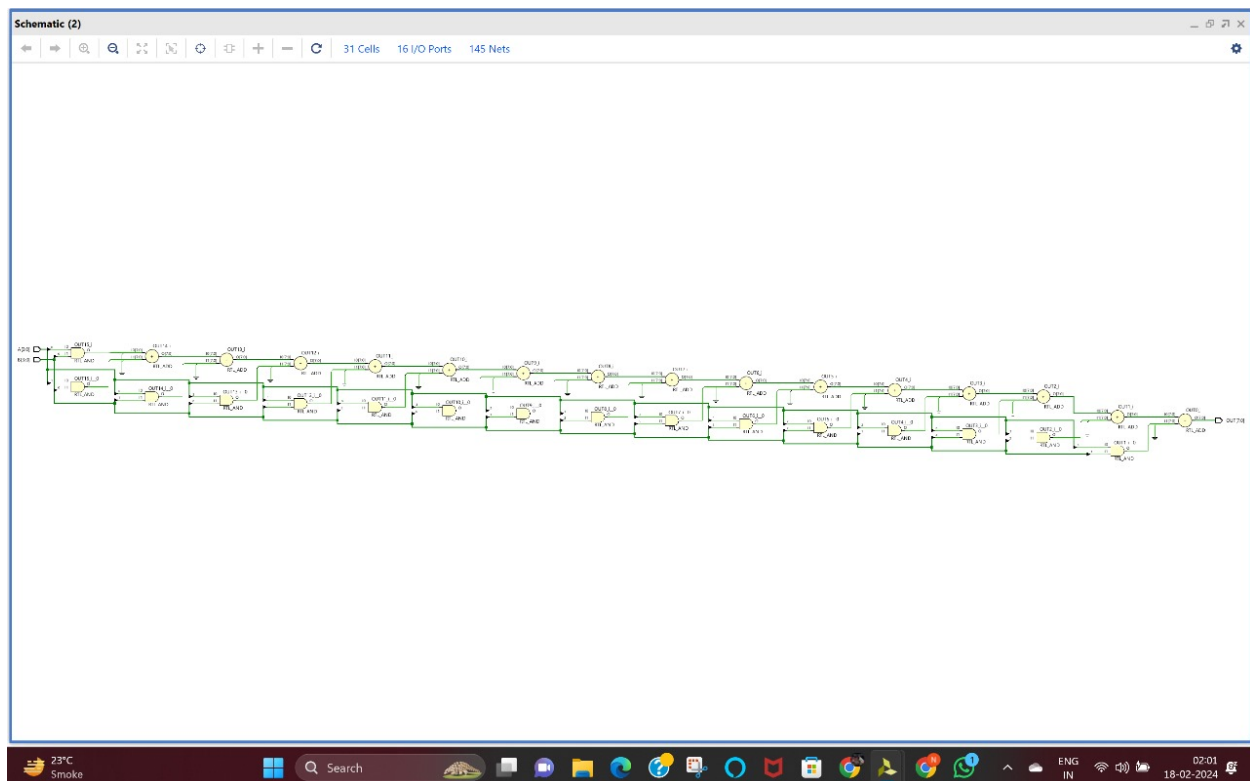

Simulation Results :

 

b. Binary Mutiplier

```
`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company:
// Engineer:
//
// Create Date: 02/17/2024 01:19:26 PM
// Design Name:
// Module Name: binary_multiplier
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
```

```

//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
////////////////////////////////////

module binary_multiplier(
    input [7:0] A,
    input [7:0] B,
    output reg [15:0] OUT
);
    parameter n = 8;
    integer i;
    reg [15:0] t;
    always @(*) begin
        OUT = 16'b0;
        for (i = 0; i < n; i = i + 1) begin
            if (B[i]) begin
                t = (A << i);
                OUT = OUT+t;
            end
        end
    end
endmodule

```

```

TestBench
TestBench
module binary_multiplier_tb();
    reg [7:0] A;
    reg [7:0] B;
    wire [15:0] OUT;


```

```


binary_multiplier uut(A,B,OUT);
A = 1; B = 1;
#10;
A = 10; B = 23;
#10;
A = 20; B = 4;
#10;
A = 127; B = 5;
#10;
A = 8; B = 45;
#10;
A = 85; B = 100;
#10;
A = 34; B = 121;
#10;
endmodule

```

Schematic:

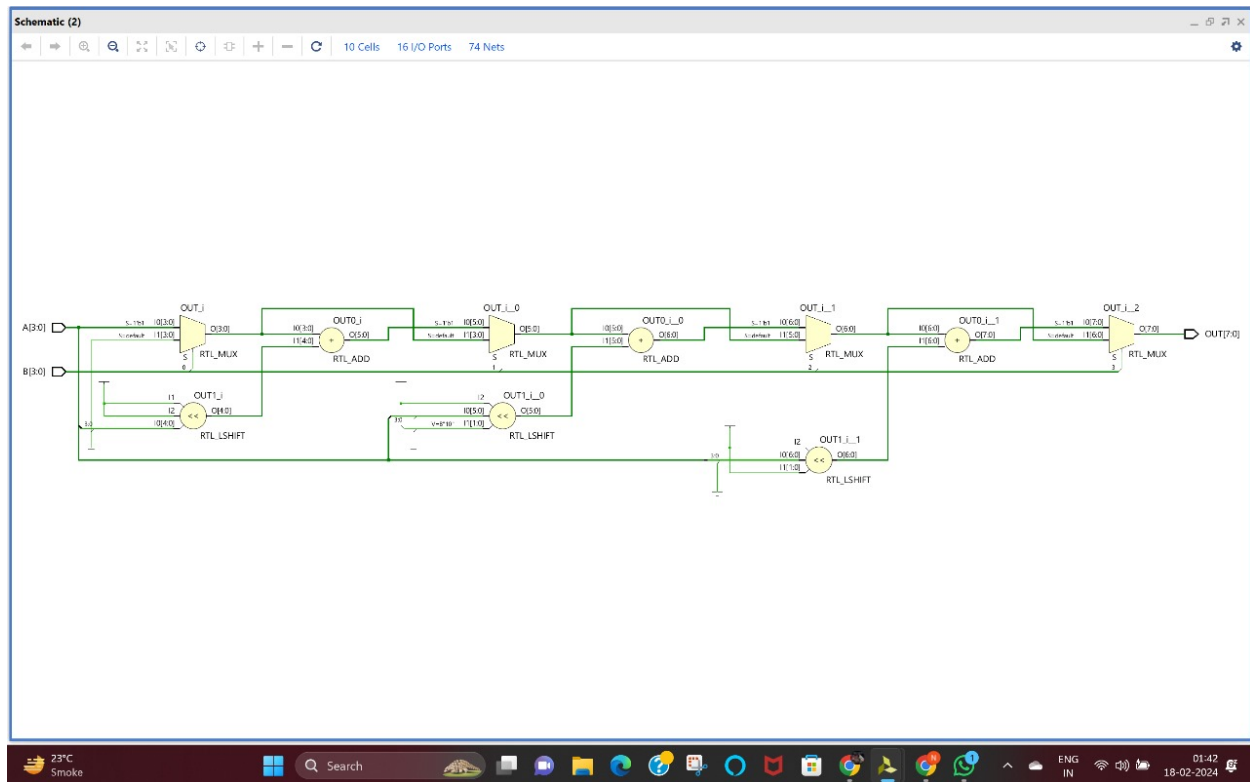



Simulations Results :

 


Comparison of a. Array multipliers and b. Binary multiplier

Power and Comparison


Array multiplier

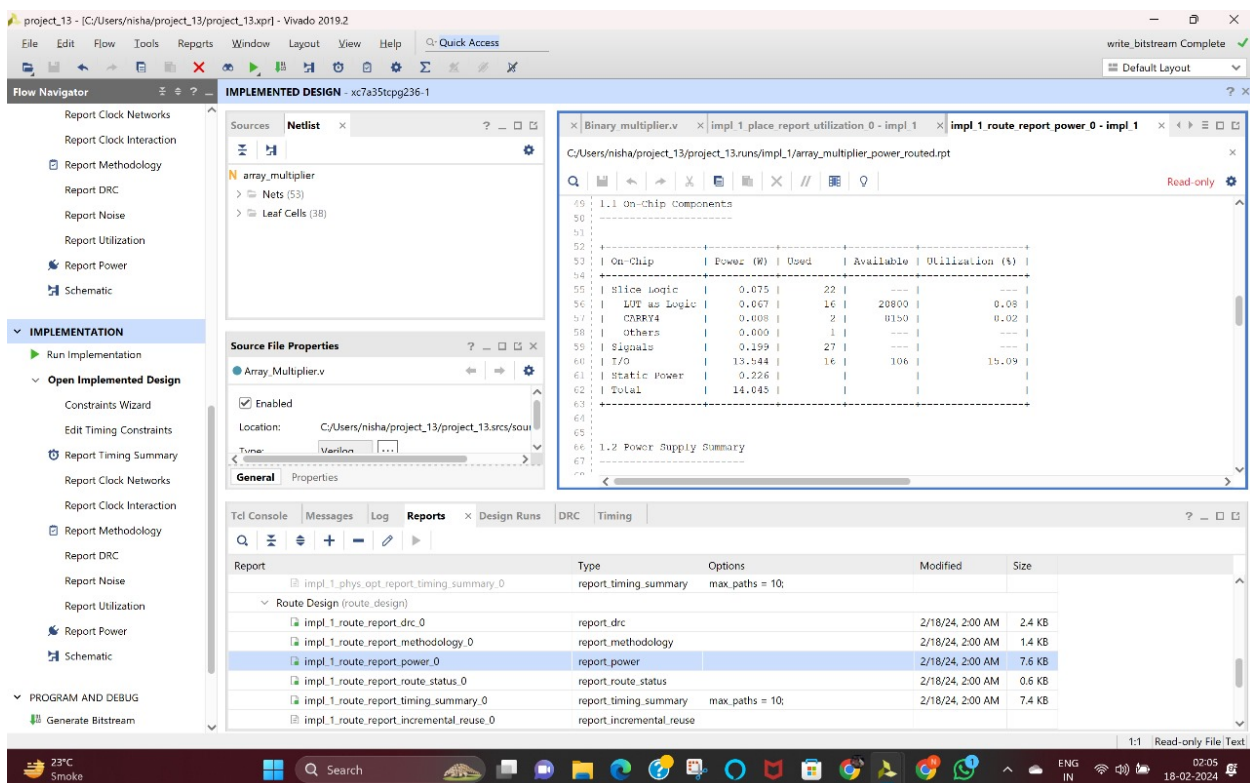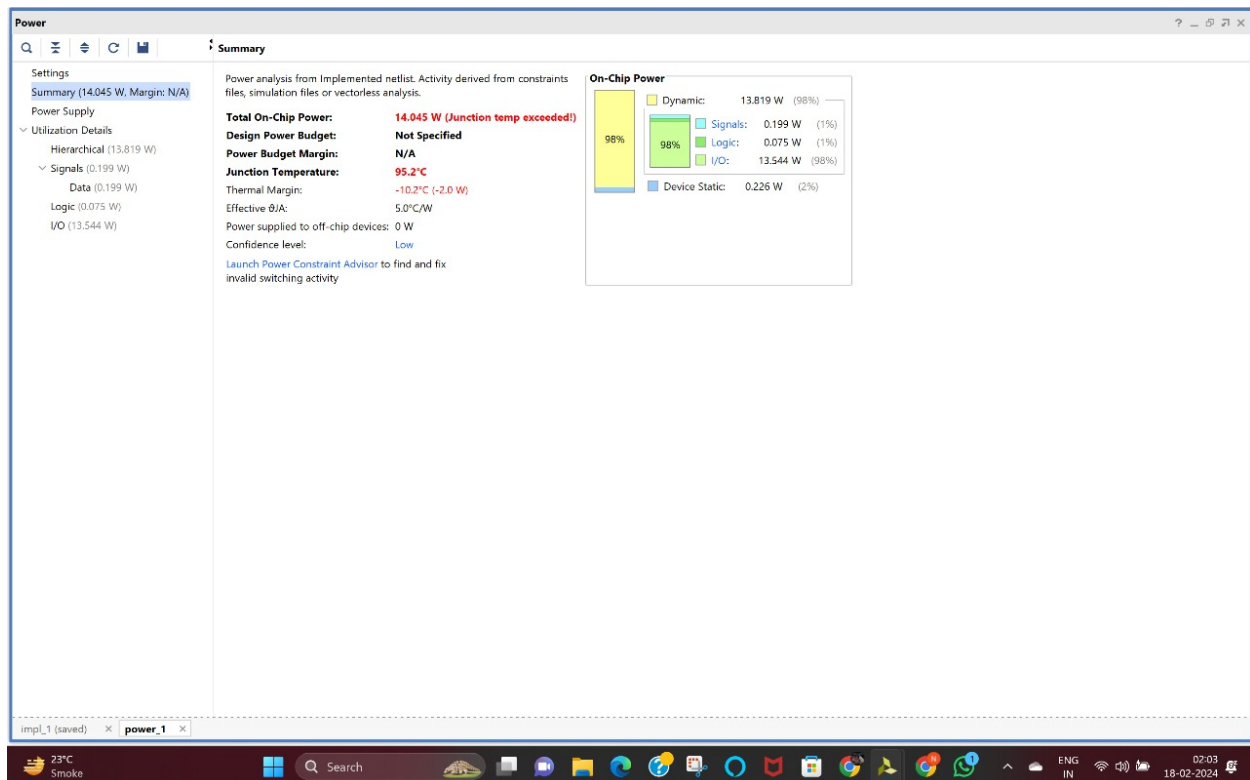

Binary multiplier

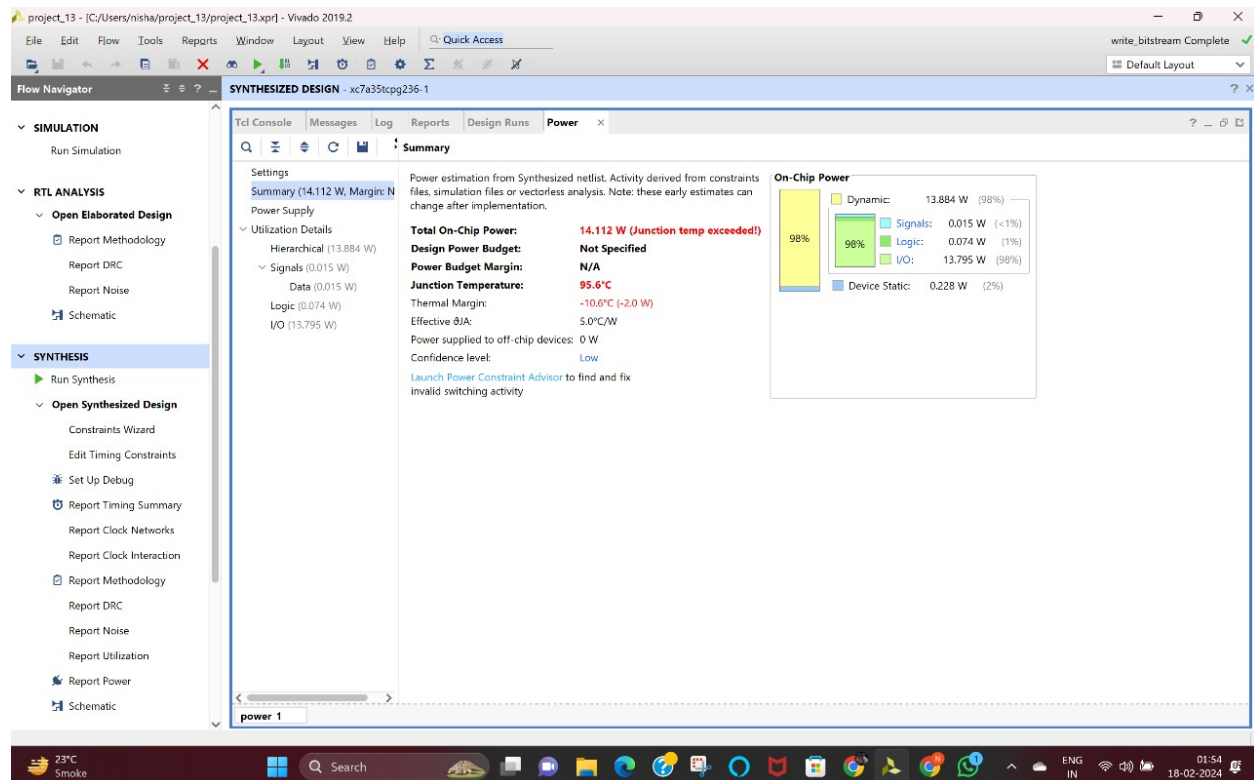

FPGA results:

 

We can see the programmed FPGA gives correct output.